

# 浙江大学

## 本科实验报告

课程名称: 数字逻辑电路设计

姓 名: 金祺书

学 院: 计算机科学与技术学院

专 业: 计算机科学与技术

指导教师: 洪奇军

报告日期: 2024 年 4 月 25 日

# 浙江大学实验报告

课程名称： 数字逻辑设计 实验类型： 综合

实验项目名称： 加法器、加减法器和 ALU 基本原理与设计

学生姓名： 金祺书 学号： 3230104248 同组学生姓名： 蒋翼泽

实验地点： 紫金港东四 509 室 实验日期： 2024 年 4 月 25 日

## 一、操作方法与实验步骤

### 1、一位全加器

根据一位全加器功能，很容易得到其真值表：


A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

根据真值表，可以获得输出  $S, C_{out}$  关于输入  $A, B, C_{in}$  的函数：

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + BC_{in} + AC_{in}$$

 使用 Logisim 绘制 Adder1b 的原理图，并将其转换成 Verilog Code




### 2、四位加减法器

在得到全加器实现后，可以为其添加一些逻辑实现加减法器。减法  $A-B$  可以看作  $A+(-B)$ ，

其中 $-B$  使用  $B$  的补码表示，即可使用全加器得到减法的结果。

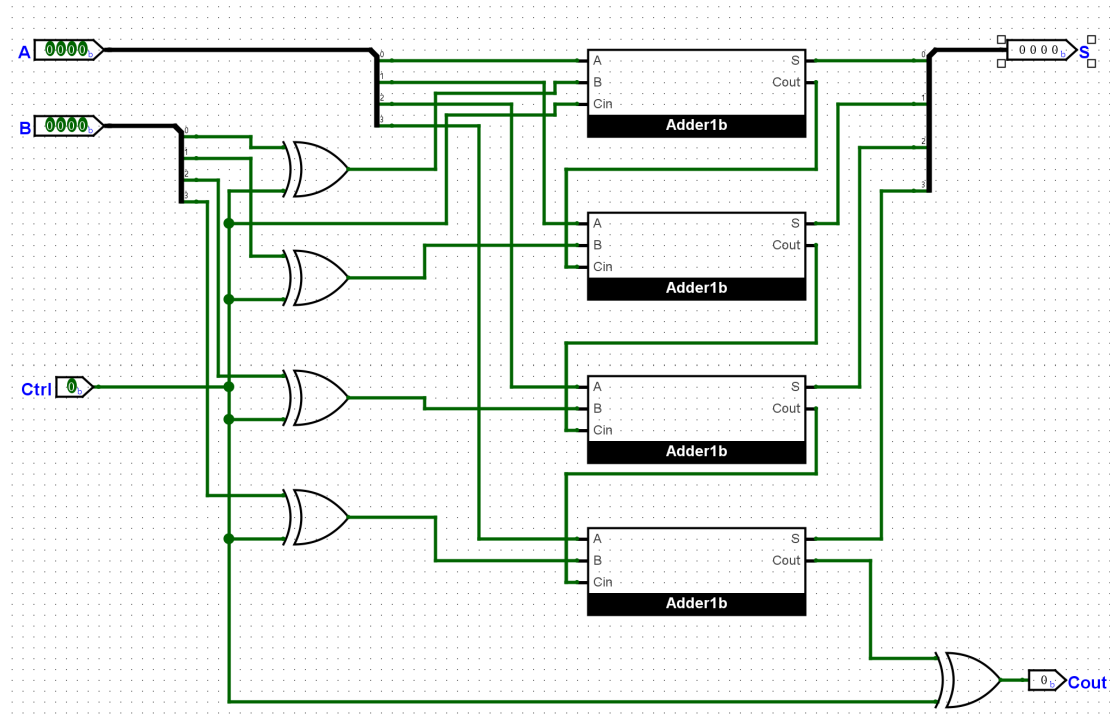
减数  $B$  的补码可以写作 $\sim B+1$ 。观察加法的  $B$  与减法的 $-B$ ，差别在于加法器第二个操作数是否取反以及是否有最低的进位，联想到异或操作的特性（一个操作数为 1 时，结果为另一个操作数的反；一个操作数为 0 时，结果与另一个操作数相同），可以得到以下原理图：



### 3、ALU 实现及应用

最后我们将实现一个简单的 4 位 ALU，进行加减法、与、或操作。

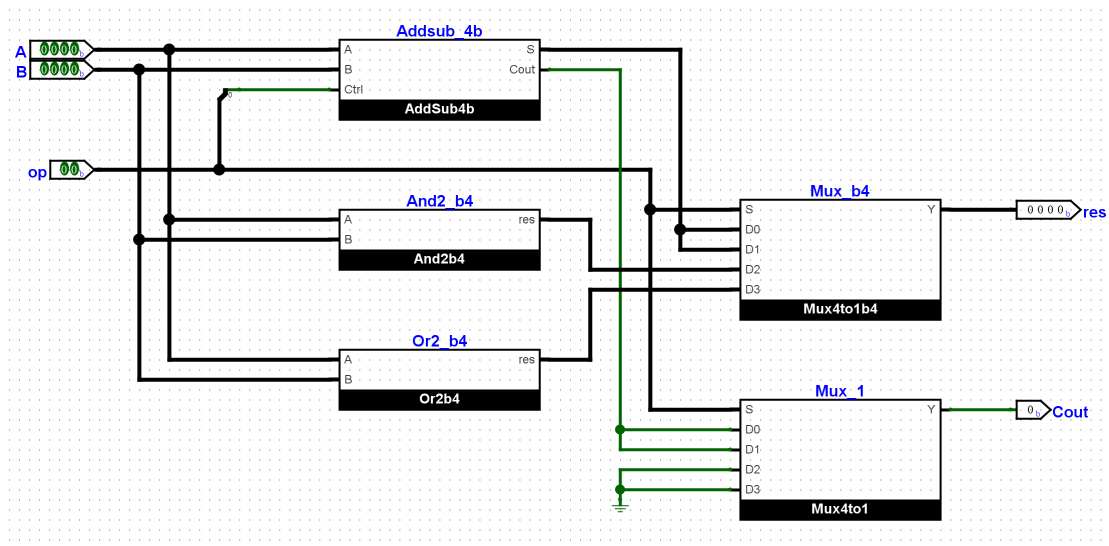(1) 使用 Logisim 绘制 ALU 的原理图，并将其转换成 Verilog Code



(2) Vivado 新建工程，对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码

如下：

```
01 `timescale 1ns / 1ps
02
```

```

03 module ALU_tb();
04 //Input
05     reg[3:0] A;
06     reg[3:0] B;
07     reg[1:0] op;
08 //Output
09     wire[3:0] res;
10     wire[1:0] Cout;
11 //Instantiate the UUT
12     ALU ALU_inst(
13         .A(A),
14         .B(B),
15         .op(op),
16         .res(res),
17         .Cout(Cout)
18     );
19     integer i;
20     initial begin
21         op=00;
22
23         A=4'b1111;
24         B=4'b0001;
25         for(i=0;i<=3;i=i+1) begin
26             {op}=i;#50;
27         end
28
29         A=4'b1000;
30         B=4'b0001;
31         for(i=0;i<=3;i=i+1) begin
32             {op}=i;#50;
33         end
34
35         A=4'b1000;
36         B=4'b0011;
37         for(i=0;i<=3;i=i+1) begin
38             {op}=i;#50;
39         end
40
41         A=4'b1000;
42         B=4'b0100;
43         for(i=0;i<=3;i=i+1) begin
44             {op}=i;#50;
45         end
46

```

```

47         A=4'b1001;
48         B=4'b0101;
49         for(i=0;i<=3;i=i+1) begin
50             {op}=i;#50;
51         end
52     end
53 endmodule

```

### (3) 添加去抖动模块

因为按键过程中会有机械原因导致的信号抖动，在 lab7 中也可以观察到，一次按下按钮数字会跳动多次。我们可以实现一个去抖动模块，当信号稳定一段时间后才更改信号值。代码如下：

```

01 module pbdebounce(
02     input wire clk,
03     input wire button,
04     output reg pbreg
05 );
06
07     reg [7:0] pbshift;
08
09     always@(posedge clk) begin
10         pbshift = pbshift<<1;
11         pbshift[0] = button;
12         if (pbshift==8'b0)
13             pbreg=0;
14         if (pbshift==8'hFF)
15             pbreg=1;
16     end
17
18 endmodule

```

### (4) 七段数码管静态显示

我们希望使用 SWORD 板上的 8 个七段数码管，它接收串行数据以减少管脚使用。我们需要一个模块将 64 位的七段数码管数据转换为 1 位串行输出以及相应的同步信号，即并转串模块 P2S，将 P2S\_io.v 和 P2S.edf 添加进工程即可，需要注意将工程中 P2S.edf 的文件格式设置为 EDIF（右键文件选择 Set file type）。

### (5) CreateNumber 模块

在本模块中使用 AddSub4b 模块，实现按键自增/自减。代码如下：

```

01 `timescale 1ns / 1ps
02

```

```

03 module Top(
04     input wire clk,
05     input wire [1:0] BTN,
06     input wire [1:0] SW1,
07     input wire [1:0] SW2,
08     input wire [11:0] SW,
09     output wire [3:0] AN,
10     output wire [7:0] SEGMENT,
11     output wire BTNX4,
12     output wire seg_clk,
13     output wire seg_clrn,
14     output wire seg_sout,
15     output wire SEG_PEN
16 );
17     wire [15:0] num;
18     wire [1:0] btn_out;
19     wire [3:0] res;
20     wire Co;
21     wire [31:0] clk_div;
22     wire [15:0] disp_hexs;
23     wire [15:0] disp_hexs_my;
24
25     assign disp_hexs[15:12] = num[7:4];           // B
26     assign disp_hexs[11:8] = num[3:0];           // A
27     assign disp_hexs[7:4] = {3'b000, Co};
28     assign disp_hexs[3:0] = res[3:0];           // C
29
30     /* Code here */
31     assign disp_hexs_my = 16'b0100_0010_0100_1000; // Fill the
last four digits of your student id in ()
32
33     assign BTNX4 = 1'b0;
34
35     clkdiv m2(.clk(clk), .rst(0), .div_res(clk_div));
36     pbdebounce
m0(.clk(clk_div[17]), .button(BTN[0]), .pbreg(btn_out[0]));
37     pbdebounce
m1(.clk(clk_div[17]), .button(BTN[1]), .pbreg(btn_out[1]));
38
39     CreateNumber m3(.btn({2'b0, btn_out}), .sw({2'b0,
SW1}), .num(num)); // Attachment
40
41     // The ALU module you wrote
42     ALU m5(    .A(num[3:0]),

```

```

43             .B(num[7:4]),                                // fill
sth. in ()
44             .op(SW2),                                    // fill sth. in
()
45             .res(res),                                    // fill sth.
in ()
46             .Cout(Co));
47
48     // Module you design in Lab7
49     DisplayNumber m6(    .clk(clk), .hexs(disps_hexs), .LEs(4'b0),
// fill sth. in ()
50                         .points(4'b0), .rst
51                         (1'b0),                                //
fill sth. in ()
52                         .AN(AN), .SEGMENT(SEGMENT));
53
54     // Attachment
55     SSeg_Dev
m7(.clk(clk), .flash(clk_div[25]), .Hexs({disps_hexs_my,
disps_hexs}), .LES(SW[11:4]),
56         .point({4'b0000,
SW[3:0]}), .rst(1'b0), .Start(clk_div[20]), .seg_clk(seg_clk),
57
        .seg_clrn(seg_clrn), .SEG_PEN(SEG_PEN), .seg_sout(seg_sout));
58
59 endmodule

```

(6) 通过约束文件:

```

01 # Filename: constraints_lab8.xdc
02 ## Constraints file for Lab8
03
04 # Main clock
05 set_property PACKAGE_PIN AC18 [get_ports clk]
06 set_property IOSTANDARD LVCMOS18 [get_ports clk]
07
08 create_clock -period 10.000 -name clk [get_ports "clk"]
09
10 # Switches as inputs
11 set_property PACKAGE_PIN AA10 [get_ports {SW[0]}]
12 set_property PACKAGE_PIN AB10 [get_ports {SW[1]}]
13 set_property PACKAGE_PIN AA13 [get_ports {SW[2]}]
14 set_property PACKAGE_PIN AA12 [get_ports {SW[3]}]
15 set_property PACKAGE_PIN Y13 [get_ports {SW[4]}]
16 set_property PACKAGE_PIN Y12 [get_ports {SW[5]}]
17 set_property PACKAGE_PIN AD11 [get_ports {SW[6]}]

```

```
18 set_property PACKAGE_PIN AD10 [get_ports {SW[7]}]
19 set_property PACKAGE_PIN AE10 [get_ports {SW[8]}]
20 set_property PACKAGE_PIN AE12 [get_ports {SW[9]}]
21 set_property PACKAGE_PIN AF12 [get_ports {SW[10]}]
22 set_property PACKAGE_PIN AE8 [get_ports {SW[11]}]
23 set_property PACKAGE_PIN AF8 [get_ports {SW1[0]}]
24 set_property PACKAGE_PIN AE13 [get_ports {SW1[1]}]
25 set_property PACKAGE_PIN AF13 [get_ports {SW2[0]}]
26 set_property PACKAGE_PIN AF10 [get_ports {SW2[1]}]
27 set_property IOSTANDARD LVCMOS15 [get_ports {SW[0]}]
28 set_property IOSTANDARD LVCMOS15 [get_ports {SW[1]}]
29 set_property IOSTANDARD LVCMOS15 [get_ports {SW[2]}]
30 set_property IOSTANDARD LVCMOS15 [get_ports {SW[3]}]
31 set_property IOSTANDARD LVCMOS15 [get_ports {SW[4]}]
32 set_property IOSTANDARD LVCMOS15 [get_ports {SW[5]}]
33 set_property IOSTANDARD LVCMOS15 [get_ports {SW[6]}]
34 set_property IOSTANDARD LVCMOS15 [get_ports {SW[7]}]
35 set_property IOSTANDARD LVCMOS15 [get_ports {SW[8]}]
36 set_property IOSTANDARD LVCMOS15 [get_ports {SW[9]}]
37 set_property IOSTANDARD LVCMOS15 [get_ports {SW[10]}]
38 set_property IOSTANDARD LVCMOS15 [get_ports {SW[11]}]
39 set_property IOSTANDARD LVCMOS15 [get_ports {SW1[0]}]
40 set_property IOSTANDARD LVCMOS15 [get_ports {SW1[1]}]
41 set_property IOSTANDARD LVCMOS15 [get_ports {SW2[0]}]
42 set_property IOSTANDARD LVCMOS15 [get_ports {SW2[1]}]
43
44 # Key as inputs
45 set_property PACKAGE_PIN W16 [get_ports BTN4]
46 set_property IOSTANDARD LVCMOS18 [get_ports BTN4]
47 set_property PACKAGE_PIN V14 [get_ports {BTN[1]}]
48 set_property IOSTANDARD LVCMOS18 [get_ports {BTN[1]}]
49 set_property PACKAGE_PIN W14 [get_ports {BTN[0]}]
50 set_property IOSTANDARD LVCMOS18 [get_ports {BTN[0]}]
51
52 set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets BTN*]
53
54 # Arduino-Segment & AN
55 set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
56 set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
57 set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
58 set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
59 set_property PACKAGE_PIN AB22 [get_ports {SEGMENT[0]}]
60 set_property PACKAGE_PIN AD24 [get_ports {SEGMENT[1]}]
61 set_property PACKAGE_PIN AD23 [get_ports {SEGMENT[2]}]
```




```
62 set_property PACKAGE_PIN Y21 [get_ports {SEGMENT[3]}]
63 set_property PACKAGE_PIN W20 [get_ports {SEGMENT[4]}]
64 set_property PACKAGE_PIN AC24 [get_ports {SEGMENT[5]}]
65 set_property PACKAGE_PIN AC23 [get_ports {SEGMENT[6]}]
66 set_property PACKAGE_PIN AA22 [get_ports {SEGMENT[7]}]
67 set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
68 set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
69 set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
70 set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
71 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[0]}]
72 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[1]}]
73 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[2]}]
74 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[3]}]
75 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[4]}]
76 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[5]}]
77 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[6]}]
78 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[7]}]
79
80 set_property PACKAGE_PIN M24 [get_ports {seg_clk}]
81 set_property IOSTANDARD LVCMOS33 [get_ports {seg_clk}]
82 set_property PACKAGE_PIN M20 [get_ports {seg_clrn}]
83 set_property IOSTANDARD LVCMOS33 [get_ports {seg_clrn}]
84 set_property PACKAGE_PIN L24 [get_ports {seg_sout}]
85 set_property IOSTANDARD LVCMOS33 [get_ports {seg_sout}]
86 set_property PACKAGE_PIN R18 [get_ports {SEG_PEN}]
87 set_property IOSTANDARD LVCMOS33 [get_ports {SEG_PEN}]
```

生成比特流下板验证。


## 二、实验结果与分析

### 1、ALU 实现及应用

Vivado 工程中的文件结构如下：

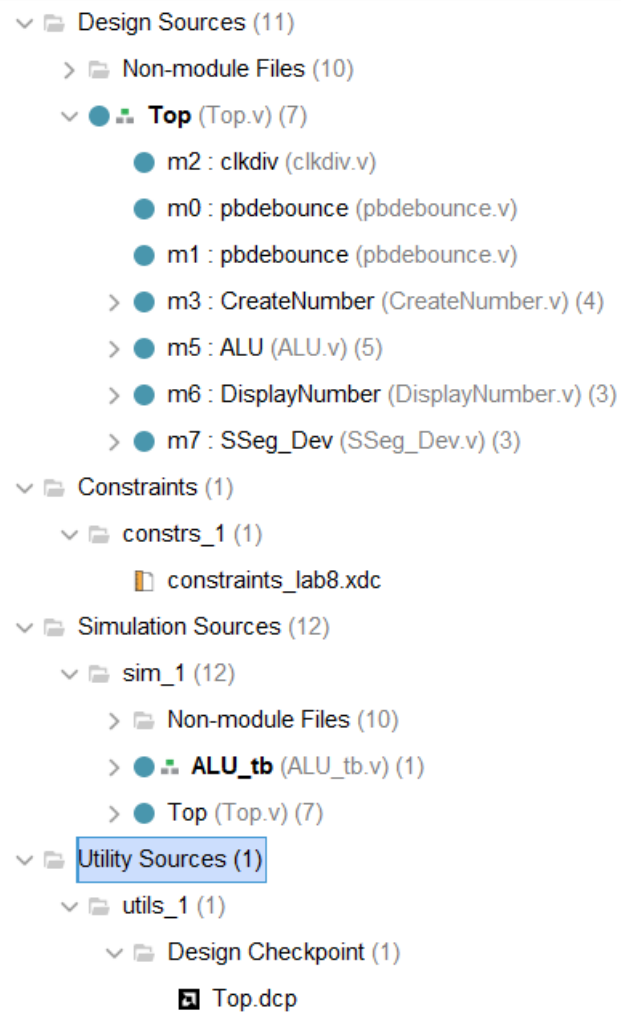


导入 Vivado 后的仿真界面截图如下：

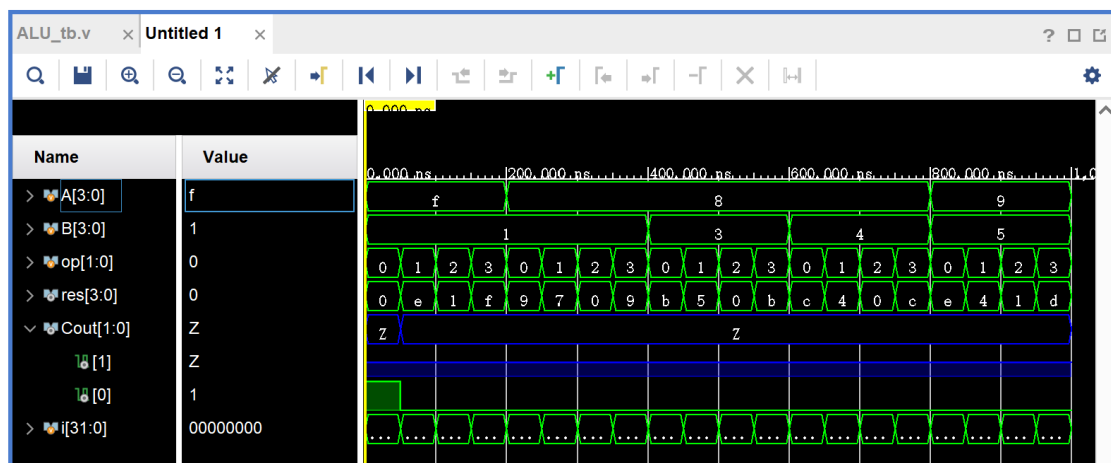

在该仿真过程中，A，B 分别代表两个参与运算的数字，op 从 0 到 3 分别代表+，-，&，|的运算符，res 则是运算结果，以 A=f，B=1 为例，A+B=0，A-B=e，A&B=1，A|B=f，仿真结果符合预期。

下板结果如下：

 

从左到右两个开关控制运算方式，00 代表+，01 代表-，10 代表按位与，11 代表按位或。两个按钮分别控制前后两个数字的自增，从 0 到 F，到 F 后再增变为 0。前四位数字为学号的后四位数字，后四位数字分别代表两个参与运算的数字，一个 0 代表等于号，最后一位数字代表运算结果，符合预期。

### 三、讨论、心得

在这次的实验过程中，原理图与仿真过程还算顺利，但是在上板时因上下两块数码管示数不一致而困扰了很久，最后在向老师寻求帮助后发现是之前 lab6 和 lab7 原理图绘制过程中接线接错没有保存正确接线导致 lab8 反复调用出错的。说明以后应当更仔细避免小错误，更应该保存每次实验的正确结果代码与原理图。

# 浙江大学

## 本科实验报告

课程名称：数字逻辑电路设计

姓 名：金祺书

学 院：计算机科学与技术学院

专 业：计算机科学与技术

指导教师：洪奇军

报告日期：2024 年 5 月 11 日

# 浙江大学实验报告

课程名称： 数字逻辑设计 实验类型： 综合

实验项目名称： 同步时序电路设计


学生姓名： 金祺书 学号： 3230104248 同组学生姓名： 蒋翼泽

实验地点： 紫金港东四 509 室 实验日期： 2024 年 5 月 9 日

## 一、操作方法与实验步骤

### 1、SR 锁存器

 (1) 使用 Logisim 绘制 SR\_latch 的原理图，并将其转换成 Verilog Code



(2) Vivado 新建工程，对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码

如下：

```
01 `timescale 1ns / 1ps
02
03 module SR_latch_tb();
04 //Inputs
05     reg S;
06     reg R;
07 //Outputs
08     wire Q;
09     wire Qbar;
10 //Instantiate the UUT
11     SR_latch SR_latch_inst (
12         .S(S),
13         .R(R),
14         .Q(Q),
15         .Qbar(Qbar)
```


```

16     );
17 //Initialize Inputs
18     initial begin
19         R=1;S=0; #50;
20         R=0;S=0; #50;
21         R=0;S=1; #50;
22         R=0;S=0; #50;
23     end
24 endmodule

```

## 2、门控 SR 锁存器

 (1) 使用 Logisim 绘制 C\_SR\_latch 的原理图，并将其转换成 Verilog Code



(2) 在 Vivado 工程中对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码如下：

下：

```

01 `timescale 1ns / 1ps
02
03 module C_SR_latch_tb();
04 //Inputs
05     reg C;
06     reg S;
07     reg R;
08 //Outputs
09     wire Q;
10     wire Qbar;
11 //Instantiate the UUT
12     C_SR_latch C_SR_latch_inst(
13         .C(C),
14         .S(S),
15         .R(R),
16         .Q(Q),
17         .Qbar(Qbar)
18     );

```

```
19 //Initialize Input
20     initial begin
21         C=1;R=1;S=0; #50;
22         R=0;S=0; #50;
23         R=0;S=1; #50;
24         R=0;S=0; #50;
25         C=0;R=1;S=0; #50;
26         R=0;S=0; #50;
27         R=0;S=1; #50;
28         R=0;S=0; #50;
29     end
30 endmodule
```

(1) 使用 Logisim 绘制 C\_D\_latch 的原理图，并将其转换成 Verilog Code

(2) 在 Vivado 工程中对该模块进行仿真激励, 检验该模块功能是否正确, 仿真激励代码如

```
01 `timescale 1ns / 1ps
02
03 module C_D_latch_tb();
04 //Inputs
05     reg C;
06     reg D;
07 //Outputs
08     wire Q;
09     wire Qbar;
10 //Instantiate the UUT
11     C_D_latch C_D_latch_inst(
12         .C(C) ,
13         .D(D) ,
14         .Q(Q) ,
15         .Qbar(Qbar)
16     );
17 //Initialize Input
```


```

18     initial begin
19         C=1;D=1; #50;
20         D=0; #50;
21         D=1; #50;
22         D=0; #50;
23         C=0;D=1; #50;
24         D=0;
25     end
26 endmodule

```

#### 4、正边沿 SR 主从触发器

 (1) 使用 Logisim 绘制 MS\_SR\_flip\_flop 的原理图，并将其转换成 Verilog Code



(2) 在 Vivado 工程中对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码如下：

下：

```

01 `timescale 1ns / 1ps
02
03 module MS_SR_flip_flop_tb();
04 //Inputs
05     reg S;
06     reg R;
07     reg clk;
08 //Outputs
09     wire Q;
10     wire Qbar;
11     wire mid_Q;
12 //Instantiate the UUT
13     MS_SR_flip_flop MS_SR_flip_flop_inst(
14         .S(S),
15         .R(R),
16         .clk(clk),
17         .Q(Q),
18         .Qbar(Qbar),
19         .mid_Q(mid_Q)
20     );
21 //Initialize Input
22     always begin
23         clk=1; #50;
24         clk=0; #50;

```



```

25     end
26     initial begin
27         R=0;S=0; #100;
28         R=0;S=1; #100;
29         R=0;S=0; #100;
30         R=1;S=0; #100;
31         R=0;S=0; #190;
32         R=0;S=1; #20;
33         R=0;S=0; #5;
34         R=1;S=0; #20;
35         R=0;S=0; #55;
36         R=0;S=1; #20;
37         R=0;S=0; #90;
38     end
39 endmodule

```

(1) 使用 Logisim 绘制 ET\_D\_flip\_flop 的原理图，并将其转换成 Verilog Code

(2) 在 Vivado 工程中对该模块进行仿真激励, 检验该模块功能是否正确, 仿真激励代码如


```
01 `timescale 1ns / 1ps
02
03 module ET_D_flip_flop_tb();
04 //Inputs
05     reg D;
06     reg clk;
07 //Outputs
08     wire Q;
09     wire Qbar;
10 //Instantiate the UUT
11     ET_D_flip_flop ET_D_flip_flop_inst(
12         .D(D) ,
13         .clk(clk) ,
14         .Q(Q) ,
15         .Qbar(Qbar)
16     );
17 //Initialize Input
18     always begin
```

```
19         clk=1; #50;
20         clk=0; #50;
21     end
22     initial begin
23         D=0; #150;
24         D=1; #150;
25         D=0; #150;
26         D=1; #150;
27     end
28 endmodule
```

## 二、实验结果与分析

### 1、SR 锁存器


导入 Vivado 后的仿真界面截图如下：

 

当 SR 为 01 时，Q 置 0；SR 为 00 时，保持上一状态；SR 为 10 时，Q 置 1，符合预期要求。

### 2、门控 SR 锁存器


导入 Vivado 后的仿真界面截图如下：

 

当 C 为 0 时，保持原有信号，RS 信号无效；当 C 为 1 时，RS 信号有效，RS=10，Q 置 0，RS=01，Q 置 1，RS=00，信号保持上一状态，符合预期要求。

### 3、门控 D 锁存器


导入 Vivado 后的仿真界面截图如下：

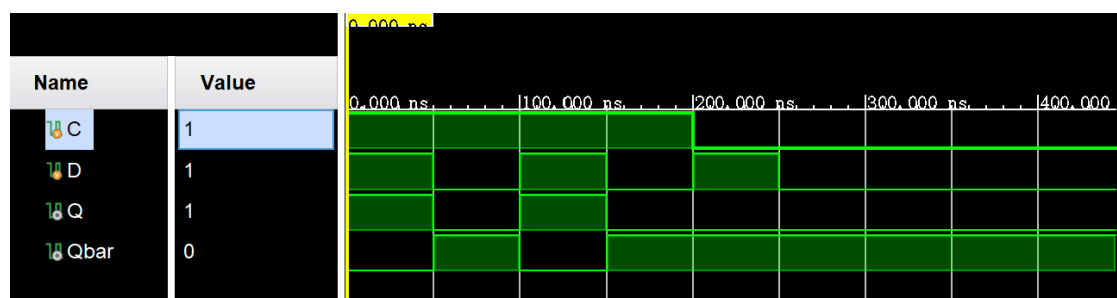

C 为 0 时，D 无效，Q 信号保持，C 为 1 时，D=1，Q 置 1，D=0，Q 置 0，符合预期要求。

#### 4、正边沿 SR 主从触发器

导入 Vivado 后的仿真界面截图如下：

 


clk 处于低位时，master 门控有效，slave 门控无效，对 D 进行修改，master 的输出会改变，但 slave 的输出（也就是触发器的输出）不会改变，clk 上升沿后一小段时间内，master 门控变为无效，slave 门控有效，master 输出不会再改变，slave 接收到 master 的输出并改变或维持自身输出。

clk 处于高位时，master 门控无效，slave 门控有效，对 D 进行修改，master 的输出不会改变，因此 slave 的输出也不会改变

但是该主从触发器存在一次性采样问题，发现 S 出现噪音信号时可能触发器的输出，如途中的 S，R 的小突起，使得输出发生了保持的变化。

#### 5、正边沿 D 触发器

导入 Vivado 后的仿真界面截图如下：

 

clk 处于低位时，不论 D 为何，输入处理阶段的两个锁存器均输出 1，输出处理阶段的锁存器保持之前的状态。clk 上升沿，输入处理阶段两个锁存器有且只有一个会输出 0，若 D 为 0，则图中靠下锁存器输出 0，若 D 为 1，则图中靠上锁存器输出 0。

clk 处于高位时，输入处理阶段的两个锁存器维持上升沿改变后的输出（即有且只有一个输出 0），且 D 的改变并不会影响锁存器的状态。

输出处理阶段的锁存器会根据输入处理的锁存器输出进行 set 或 reset，即改变或维持触发器的输出。

### 三、讨论、心得

本次实验较为简单，很快速就完成了，应当继续保持对此的熟悉程度。

# 浙江大学

## 本科实验报告

课程名称: 数字逻辑电路设计

姓 名: 金祺书

学 院: 计算机科学与技术学院

专 业: 计算机科学与技术

指导教师: 洪奇军

报告日期: 2024 年 5 月 11 日

# 浙江大学实验报告

课程名称：数字逻辑设计 实验类型：综合

实验项目名称：同步时序电路设计

学生姓名：金祺书 学号：3230104248 同组学生姓名：蒋翼泽

实验地点：紫金港东四 509 室 实验日期：2024 年 5 月 11 日

## 一、操作方法与实验步骤

### 1、四位同步二进制计数器

四位二进制计数器输入时钟信号，输出为四位二进制值，二进制值从高位到低位分别是  $Q_d, Q_c, Q_b, Q_a$ 。每一个时钟信号的上升沿， $\{Q_d, Q_c, Q_b, Q_a\}$  的值就自增。根据功能描述，可以得到真值表及卡诺图如下，其中  $Q$  表示当前状态（输出）， $D$  表示下一状态（下一个时钟上升沿到来后的输出）：

	$Q_A$	$Q_B$	$Q_C$	$Q_D$	$D_A$	$D_B$	$D_C$	$D_D$
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
10	0	1	0	1	1	1	0	1
11	1	1	0	1	0	0	1	1
12	0	0	1	1	1	0	1	1
13	1	0	1	1	0	1	1	1
14	0	1	1	1	1	1	1	1
15	1	1	1	1	0	0	0	0

1	0	0	1
1	0	0	1
1	0	0	1
1	0	0	1

$D_A$

0	1	0	1
0	1	0	1
0	1	0	1
0	1	0	1

$D_B$

0	0	1	0
1	1	0	1
1	1	0	1
0	0	1	0

D<sub>C</sub>

0	0	0	0
0	0	1	0
1	1	0	1
1	1	1	1

D<sub>D</sub>


由卡诺图可以化简得到激励函数如下：

$$\begin{aligned}
 D_A &= \overline{Q_A} \\
 D_B &= \overline{Q_A}Q_B + Q_A\overline{Q_B} = \overline{Q_A \oplus Q_B} \\
 D_C &= \overline{Q_B}Q_C + \overline{Q_A}Q_C + Q_AQ_B\overline{Q_C} = \overline{Q_A}\overline{Q_B}Q_C + Q_AQ_B\overline{Q_C} = \overline{Q_AQ_B \oplus Q_C} = \overline{\overline{Q_A} + \overline{Q_B} \oplus Q_C} \\
 D_D &= \overline{Q_B}Q_D + \overline{Q_A}Q_D + \overline{Q_C}Q_D + Q_AQ_BQ_C\overline{Q_D} = \overline{Q_A}\overline{Q_B}\overline{Q_C}Q_D + Q_AQ_BQ_C\overline{Q_D} = \overline{Q_AQ_BQ_C \oplus Q_D} \\
 &= \overline{\overline{Q_A} + \overline{Q_B} + \overline{Q_C} \oplus Q_D}
 \end{aligned}$$

进位发生在四位数据均为 1 时，因此可以得到：

$$R_C = Q_AQ_BQ_CQ_D = \overline{\overline{Q_A} + \overline{Q_B} + \overline{Q_C} + \overline{Q_D}}$$

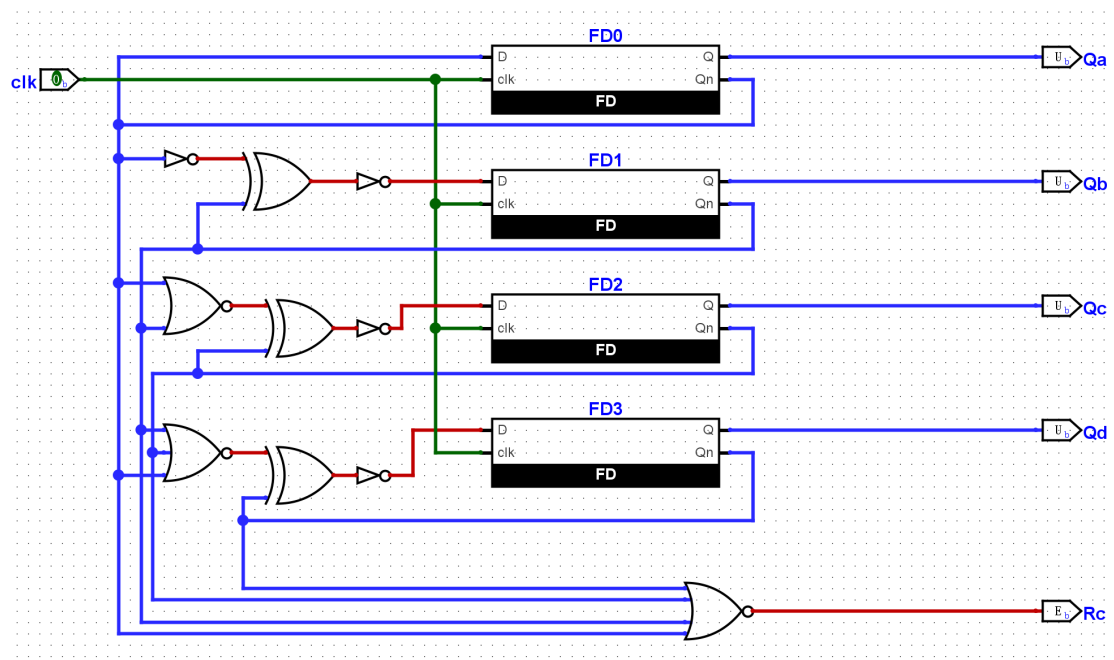(1) 使用 Logisim 绘制 Counter4b 的原理图，并将其转换成 Verilog Code



(2) 电路图上的 FD 为 D 触发器，但我们只需要在 Logisim 中画一个“空壳”即可，导出

Verilog 代码后，将 FD.v 中的内容替换如下：

```

01 module FD(
02     input clk,
03     input D,
04     output Q,
05     output Qn
06 );
07
08     reg Q_reg = 1'b0;

```

```

09     always @(posedge clk) begin
10         Q_reg <= D;
11     end
12
13     assign Q = Q_reg;
14     assign Qn = ~Q_reg;
15
16 endmodule

```

(3) Vivado 新建工程，对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码

如下：

```

01 `timescale 1ns / 1ps
02 module Counter4b_tb();
03 //Input
04     reg clk;
05 //Outputs
06     wire Qa;
07     wire Qb;
08     wire Qc;
09     wire Qd;
10     wire Rc;
11 //Instantiate the UUT
12     Counter4b Counter4b_inst(
13         .clk(clk),
14         .Qa(Qa),
15         .Qb(Qb),
16         .Qc(Qc),
17         .Qd(Qd),
18         .Rc(Rc)
19     );
20 //Initialize Input
21     always begin
22         clk=0; #10;
23         clk=1; #10;
24     end
25 endmodule

```

(4) 导出 Verilog 代码，顶层代码 Top 如下：

```

01 module Top(
02     input wire clk,
03     output wire LED,
04     output wire [7:0] SEGMENT,
05     output wire [3:0] AN
06 );

```



```

07
08     wire Qa;
09     wire Qb;
10     wire Qc;
11     wire Qd;
12     wire [3:0] Hex;
13
14     /* module clk_1s at submodules/clk_1s.v */
15     clk_1s m0(.clk(clk), .clk_1s(clk_1s));
16
17     /* You need to implement module Counter4b */
18     Counter4b
19 m1(.clk(clk_1s), .Qa(Qa), .Qb(Qb), .Qc(Qc), .Qd(Qd), .Rc(LED));
20
21     assign Hex = {Qd, Qc, Qb, Qa};
22
23     // Please replace module below with your module completed in
24 Lab 6
25
26     // Pay attention to the correctness of the module name and
27 port name
28
29     // NOTE: SEGMENT and Segement are different port names
30
31     // BTN[0]: LE, valid with value 0
32     // BTN[1]: point, light with value 1
33     // SW[7:4]: AN, light with value 1 (AN[i] = ~SW[i+4])
34     // SW[3:0]: number to display
35     DispNum display(.BTN(2'b00), .SW({4'b0001,
36 Hex}), .SEGMENT(SEGMENT), .AN(AN));
37
38 endmodule

```

子模块 clk\_1s 代码如下:

```

01 `timescale 1ns / 1ps
02
03 module clk_1s(
04     input clk,
05     output reg clk_1s
06 );
07
08     reg [31:0] cnt;
09
10     initial begin
11         cnt = 32'b0;
12     end
13

```

```

14     wire[31:0] cnt_next;
15     assign cnt_next = cnt + 1'b1;
16
17     always @(posedge clk) begin
18         if(cnt<50_000_000)begin
19             cnt <= cnt_next;
20         end
21         else begin
22             cnt <= 0;
23             clk_1s <= ~clk_1s;
24         end
25     end
26
27 endmodule

```

通过约束文件：

```

01 # Filename: constraints_labA_part1.xdc
02 ## Constraints file for LabA-part1
03
04 # Main clock
05 set_property PACKAGE_PIN AC18 [get_ports clk]
06 set_property IOSTANDARD LVCMOS18 [get_ports clk]
07
08 create_clock -period 10.000 -name clk [get_ports "clk"]
09
10 # LED
11 set_property PACKAGE_PIN AF24 [get_ports {LED}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {LED}]
13
14 set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
15 set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
16 set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
17 set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
18 set_property PACKAGE_PIN AB22 [get_ports {SEGMENT[0]}]
19 set_property PACKAGE_PIN AD24 [get_ports {SEGMENT[1]}]
20 set_property PACKAGE_PIN AD23 [get_ports {SEGMENT[2]}]
21 set_property PACKAGE_PIN Y21 [get_ports {SEGMENT[3]}]
22 set_property PACKAGE_PIN W20 [get_ports {SEGMENT[4]}]
23 set_property PACKAGE_PIN AC24 [get_ports {SEGMENT[5]}]
24 set_property PACKAGE_PIN AC23 [get_ports {SEGMENT[6]}]
25 set_property PACKAGE_PIN AA22 [get_ports {SEGMENT[7]}]
26 set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
27 set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
28 set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
29 set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]

```

```

30 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[0]}]
31 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[1]}]
32 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[2]}]
33 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[3]}]
34 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[4]}]
35 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[5]}]
36 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[6]}]
37 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[7]}]

```

生成比特流下板验证。

## 2、十六位可逆同步二进制计数器

与“四位可逆同步二进制计数器”相比，十六位可逆同步二进制计数器拓展位宽到 16 位，且添加了一个控制信号 s 用来选择“自增”或“自减”。计数器功能如下：

- ①在时钟上升沿对输出 cnt 进行修改；当 s=0 时进行自增，s=1 时进行自减。
- ②同步重置信号 rst 高位有效，即在时钟上升沿时若 rst=1 才进行重置，重置时将 cnt 修改为 0。
- ③非饱和计数，当前计数若为 16'hFFFF 则自增后为 16'h0；当前计数若为 16'h0 则自减后为 16'hFFFF。

(1) 设计模块 RevCounter 代码如下：

```

01 `timescale 1ns / 1ps
02
03 module RevCounter(
04     input wire clk,
05     input wire rst,
06     input wire s,
07     output reg [15:0] cnt=0,
08     output wire Rc
09 );
10     assign Rc=(~s & (~|cnt)) | (s & (&cnt));
11     always@(posedge clk) begin
12         if(rst==1)
13             cnt=0;
14         if(s==0)
15             cnt<=cnt+1;
16         else
17             cnt<=cnt-1;
18     end
19 endmodule

```

(2) 在 Vivado 工程中对该模块进行仿真激励，检验该模块功能是否正确，仿真激励代码如下：

```

01 `timescale 1ns / 1ps
02
03 module RevCounter_tb();
04 //Inputs

```

```

05     reg clk;
06     reg rst;
07     reg s;
08     //Outputs
09     wire[15:0] cnt;
10     wire Rc;
11     //Instantiate the UUT
12     RevCounter RevCounter_inst(
13         .clk(clk),
14         .rst(rst),
15         .s(s),
16         .cnt(cnt),
17         .Rc(Rc)
18     );
19     //Initialize Input
20     initial begin
21         s=1'b0;
22         rst=0; #93;
23         rst=1; #5;
24         rst=0; #101;
25         s=1'b1; #101;
26     end
27     always begin
28         clk=1'b0; #5;
29         clk=1'b1; #5;
30     end
31 endmodule

```

(3) 导出 Verilog 代码，顶层代码 Top 如下：

```

01 `timescale 1ns / 1ps
02
03 module Top(
04     input wire clk,
05     input wire [1:0] SW,
06     output wire LED,
07     output wire [7:0] SEGMENT,
08     output wire [3:0] AN
09 );
10
11     wire[15:0] cnt;
12     wire [3:0] Hex;
13     wire clk_1s;
14
15     /* module clk_100ms at submodules/clk_1s.v */
16     clk_1s clk_div_1s (.clk(clk), .clk_1s(clk_1s));

```

```

17
18     /* You need to implement module RevCounter */
19     RevCounter
counter(.clk(clk_1s), .rst(SW[1]), .s(SW[0]), .cnt(cnt), .Rc(LED));
20
21     // Please replace module below with your module completed in
Lab **7**
22     // import submodules for module DisplayNumber from your prev.
project
23     DisplayNumber
display(.clk(clk), .rst(1'b0), .hexs(cnt), .LEs(4'b0000), .points(4'b
0000), .AN(AN), .SEGMENT(SEGMENT));
24
25 endmodule

```

通过约束文件:

```

01 # Filename: constraints_labA_part1.xdc
02 ## Constraints file for LabA-part1
03
04 # Main clock
05 set_property PACKAGE_PIN AC18 [get_ports clk]
06 set_property IOSTANDARD LVCMOS18 [get_ports clk]
07
08 create_clock -period 10.000 -name clk [get_ports "clk"]
09
10 set_property PACKAGE_PIN AA10 [get_ports {SW[0]}]
11 set_property PACKAGE_PIN AB10 [get_ports {SW[1]}]
12 set_property IOSTANDARD LVCMOS15 [get_ports {SW[0]}]
13 set_property IOSTANDARD LVCMOS15 [get_ports {SW[1]}]
14
15
16 # LED
17 set_property PACKAGE_PIN AF24 [get_ports {LED}]
18 set_property IOSTANDARD LVCMOS33 [get_ports {LED}]
19
20 set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
21 set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
22 set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
23 set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
24 set_property PACKAGE_PIN AB22 [get_ports {SEGMENT[0]}]
25 set_property PACKAGE_PIN AD24 [get_ports {SEGMENT[1]}]
26 set_property PACKAGE_PIN AD23 [get_ports {SEGMENT[2]}]
27 set_property PACKAGE_PIN Y21 [get_ports {SEGMENT[3]}]
28 set_property PACKAGE_PIN W20 [get_ports {SEGMENT[4]}]
29 set_property PACKAGE_PIN AC24 [get_ports {SEGMENT[5]}]

```

```

30 set_property PACKAGE_PIN AC23 [get_ports {SEGMENT[6]}]
31 set_property PACKAGE_PIN AA22 [get_ports {SEGMENT[7]}]
32 set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
33 set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
34 set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
35 set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
36 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[0]}]
37 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[1]}]
38 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[2]}]
39 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[3]}]
40 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[4]}]
41 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[5]}]
42 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[6]}]
43 set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[7]}]


```

生成比特流下板验证。

## 二、实验结果与分析


### 1、四位同步二进制计数器


导入 Vivado 后的仿真界面截图如下：

 

可以看到，只有当 clk 上升沿时， $\{Q_A, Q_B, Q_C, Q_D\}$  实现自增，在最后  $\{Q_A, Q_B, Q_C, Q_D\} = 4'b1111$  时且 clk 上升沿时 Rc 置 1，仿真结果符合预期。

下板结果如下图：

 


 

可以看到，当比特流下载后，数字面板上从 0 开始自增，符合预期要求。

## 2、十六位可逆同步二进制计数器

导入 Vivado 后的仿真界面截图如下：

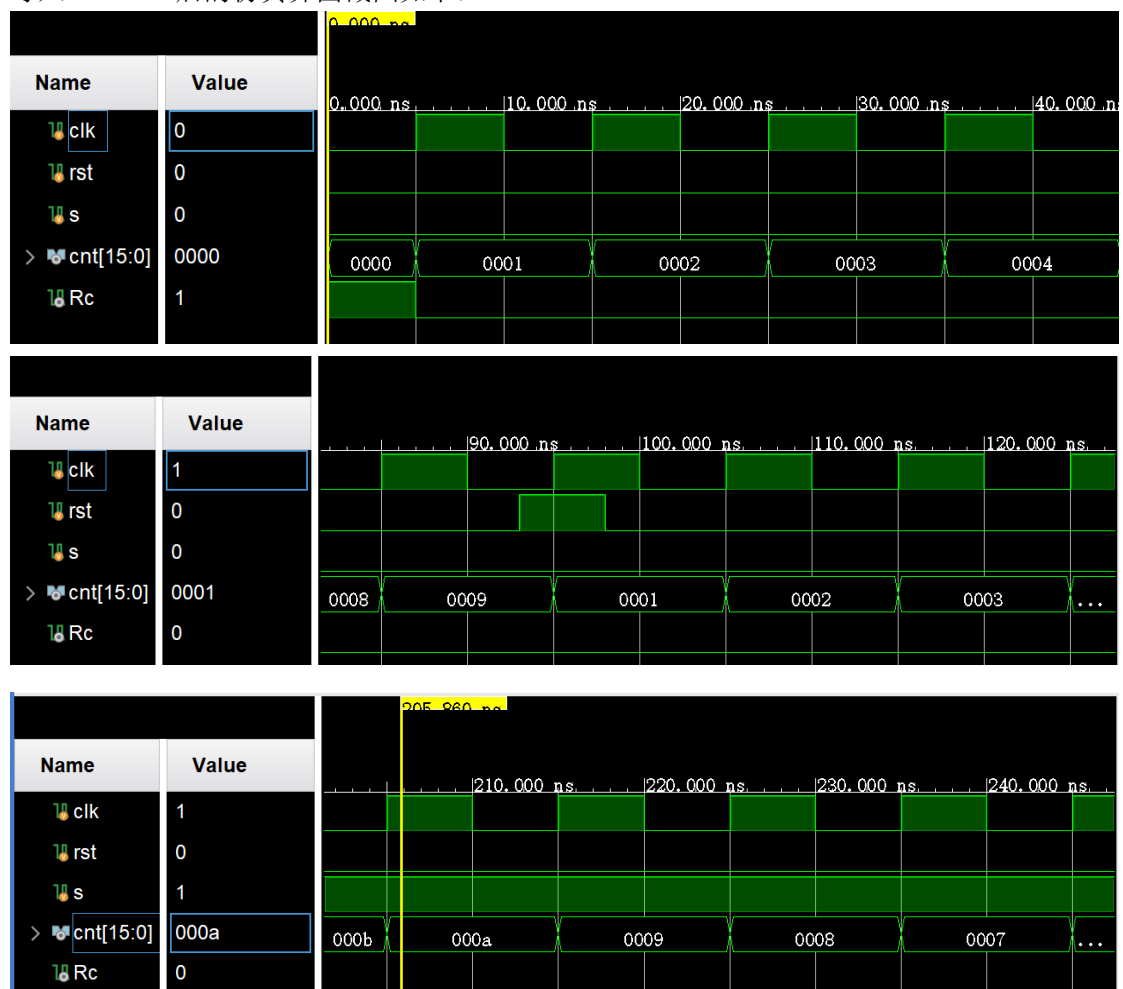

可以看到，在  $rst=0, s=0$  时，cnt 实现自增； $s=1$  时 cnt 实现自减。 $rst=1$  时，cnt 实现复位，由仿真代码可知复位立马执行自增操作，所以在仿真界面上展示的则是复位为 1，符合预期要求。

### 三、讨论、心得

本次实验有了 lab9 的经验与铺垫整体较为顺利，下板之后的结果也一次就成功符合预期，接下来应当保持，为期末大程做准备。